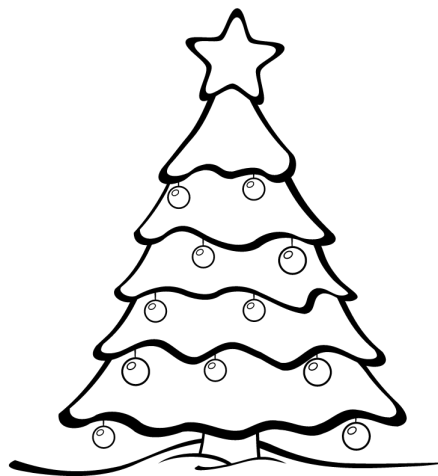


Winter Holiday Paper Circuit Templates



Joyous
KWANZAA



Happy
HANUKKAH



THANK YOU!

Thank you for downloading a Vivify product! If you have any questions, please email us at info@vivifsystem.com.

Terms of Use

All pages of this packet are copyrighted. You may not create anything to sell or share based on this packet. This packet is for one classroom use only. If others like this lesson, please direct them to the Vivify TpT Store at www.teacherspayteachers.com/Store/Vivify or to www.vivifsystem.com. You are welcome to share the cover image of this packet on your blog or via social media as long as you link back to the original product link.

ABOUT VIVIFY

Vivify is a K-12 STEM education resource company founded by two aerospace engineers, Natasha and Claire, with a passion for providing access to quality STEM education.




Our philosophy is that STEM transforms classrooms into an exciting world of curiosity, problem-solving, and creativity. STEM education can be an empowering interdisciplinary approach that brings math, science, and engineering concepts to life through challenging opportunities that mimic the complexities and excitement of the real world.

Every teacher or parent can incorporate STEM into their classroom or home given the right resources, and that is where Vivify comes in! We love creating STEM materials and are excited to bring STEM to more classrooms and homes! [Click here to learn more about Vivify.](#)



Connect with us for free STEM resources!

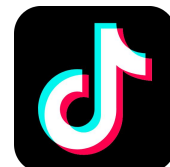Subscribe to our newsletter and receive access to a library of [free](https://www.vivifsystem.com) STEM resources through www.vivifsystem.com. Follow us on social media or listen to “[The STEM Space](#)” podcast for more resources and ideas.



Follow us for more STEM! [@vivifsystem](https://www.instagram.com/vivifsystem)


[Click here for editable link of circuit templates.](#)

Christmas is a holiday celebrated on December 25th by people around the world with both religious and secular traditions and practices for thousands of years. Popular customs include gift giving, decorating evergreen trees, special religious occasions, meals with family and friends and many around the world can be found patiently waiting for Santa Claus!

Learn more about Christmas at <https://kids.nationalgeographic.com/celebrations/article/christmas>




www.vivifystem.com

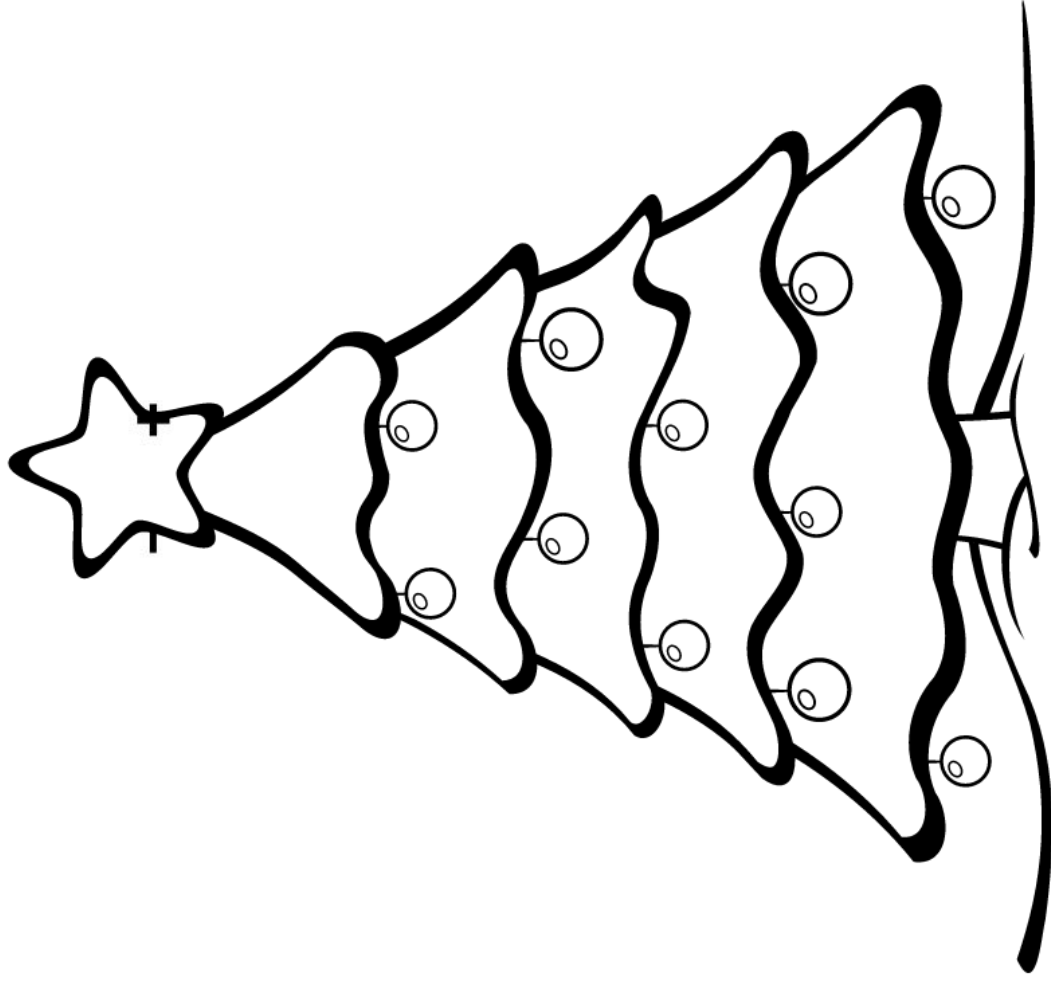

Merry Christmas!

Ghost Circuit Instructions:

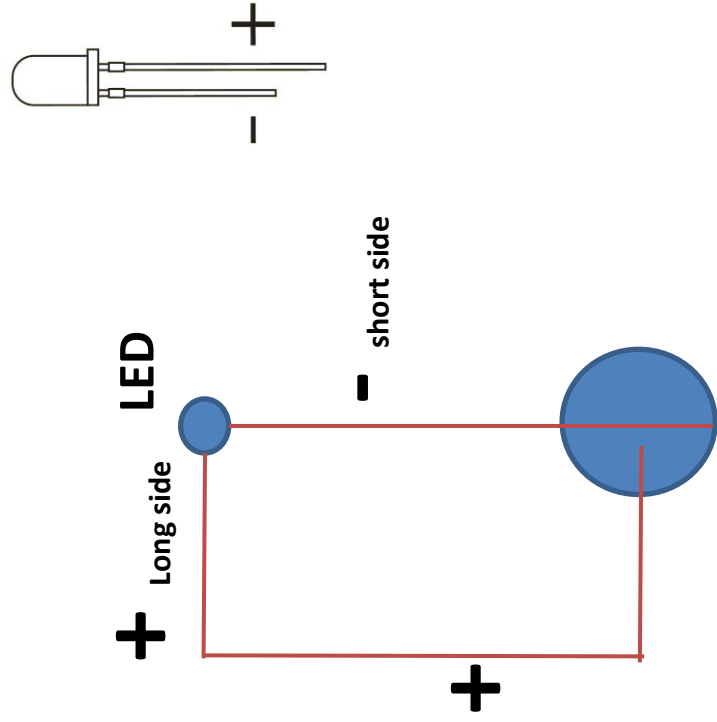1. You need: 1 LED light, copper tape, 1 battery
2. On the diagram to the left, place copper tape along all the lines on the (-) negative side. Make sure there are not breaks in the tape.
3. Place the battery negative side down where shown. Make sure it overlaps the copper tape.
4. Add copper tape to the positive (+) side of the circuit diagram all the way to the positive side of battery. Make sure to continue tape to cover battery.
5. Insert LED through the **FRONT** of the card with the longer wire (+) to the left. On inside of card, bend wires so the bulb is flat to the paper and the wires lay on top of the copper tape.
6. Add copper tape on top of the wires to secure.
7. Close card and press on "Happy Halloween." If your LED lights up, you are creating a closed circuit that allows electricity to pass from the battery to the LED!



+ *Positive side of battery:* Facing up with the + copper tape on top


- *Negative side of battery:* Facing down covering the - copper tape


Battery

Positive side of battery: Facing up with the + copper tape on top

Troubleshooting

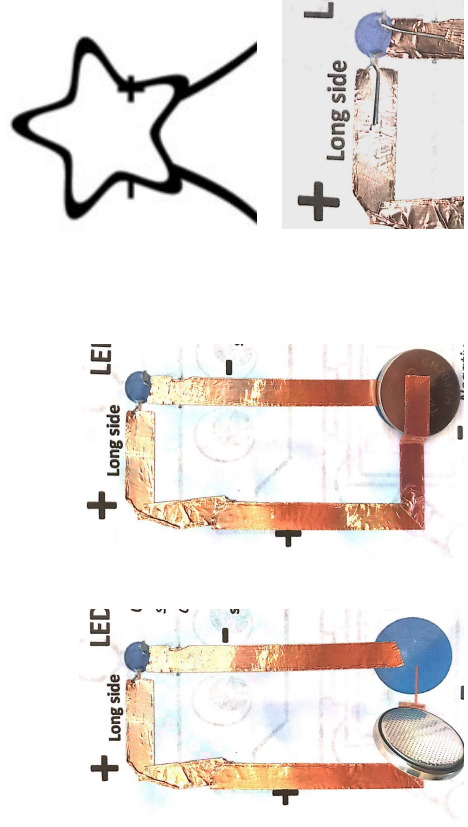1. Check LED and battery are working
2. Reverse battery
3. Make sure + and - copper tape strips are not touching
4. Make sure copper tape is continuous and smooth



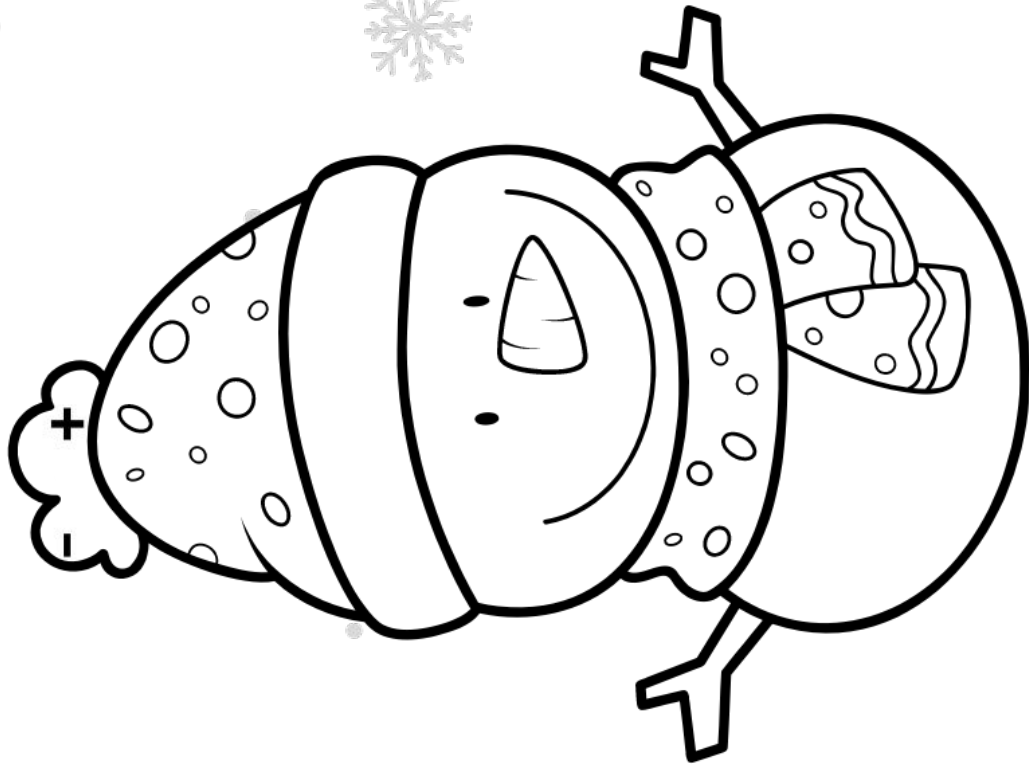


Happy Holidays!



www.vivifystem.com

Ghost Circuit Instructions:

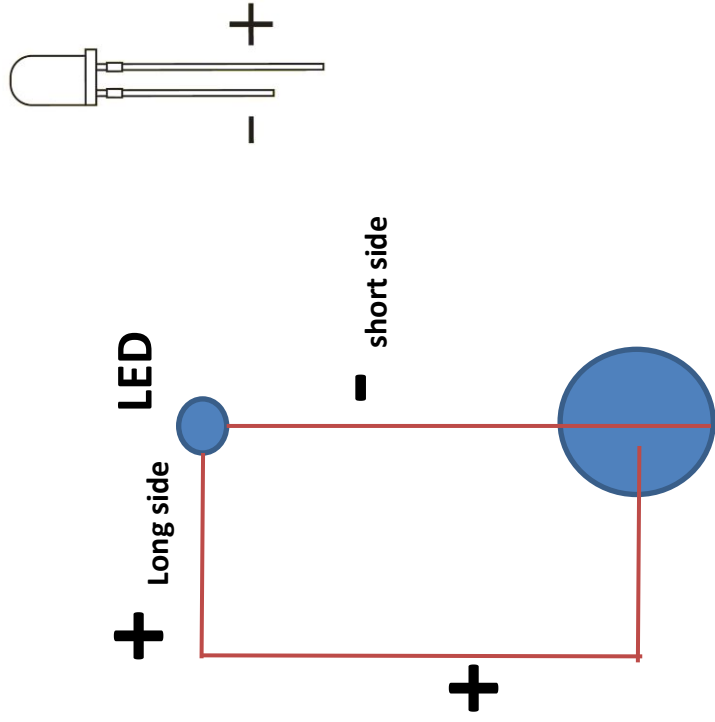1. You need: 1 LED light, copper tape, 1 battery
2. On the diagram to the left, place copper tape along all the lines on the (-) negative side. Make sure there are not breaks in the tape.
3. Place the battery negative side down where shown. Make sure it overlaps the copper tape.
4. Add copper tape to the positive (+) side of the circuit diagram all the way to the positive side of battery. Make sure to continue tape to cover battery.
5. Insert LED through the **FRONT** of the card with the longer wire (+) to the left. On inside of card, bend wires so the bulb is flat to the paper and the wires lay on top of the copper tape.
6. Add copper tape on top of the wires to secure.
7. Close card and press on "Happy Halloween." If your LED lights up, you are creating a closed circuit that allows electricity to pass from the battery to the LED!




- *Negative side of battery:*
Facing down covering the -
copper tape

Battery

Positive side of battery: Facing
up with the + copper tape on
top

Troubleshooting

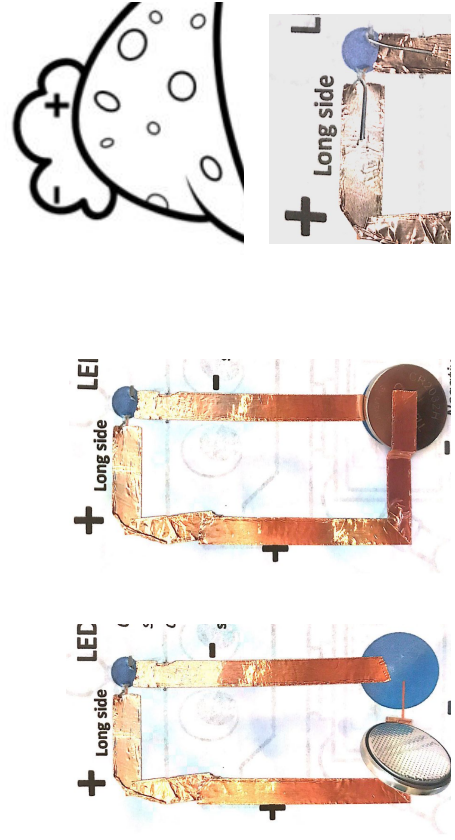1. Check LED and battery are working
2. Reverse battery
3. Make sure + and - copper tape strips are not touching
4. Make sure copper tape is continuous and smooth




Hanukkah (also spelled Chanukah) is a Jewish holiday that is also known as the “Festival of Lights” and celebrates an miraculous event from over 2,000 years ago. Hanukkah usually starts in late November to mid-December and is celebrated with special foods, family, and the lighting of a candle on the menorah on each of the eight nights.

Learn more about Hanukkah at <https://kids.nationalgeographic.com/celebrations/article/hanukkah>





www.vivifystem.com

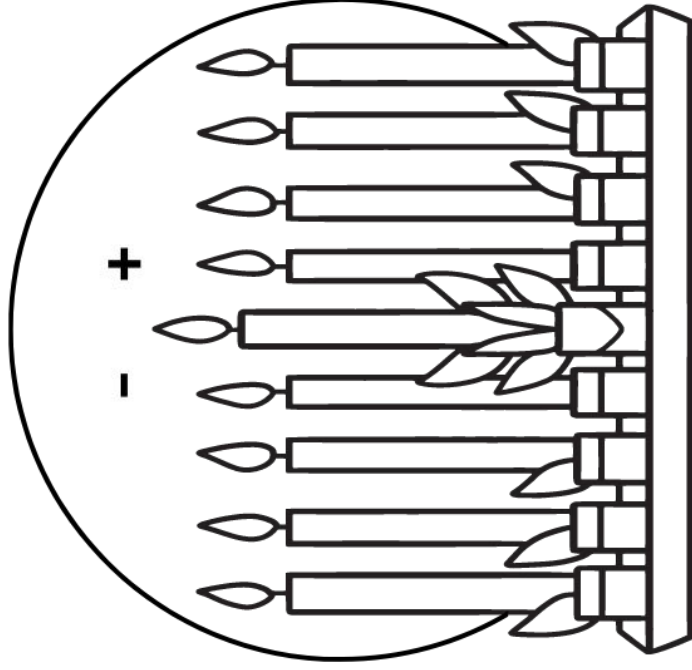

Happy
HANUKKAH

Spider Circuit Instructions:

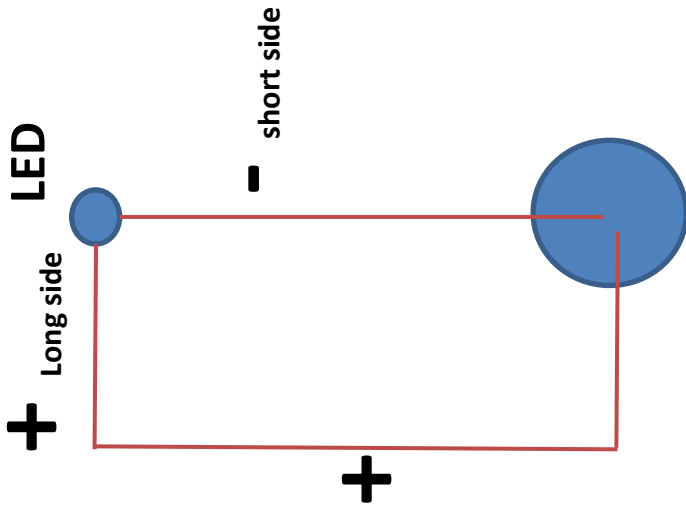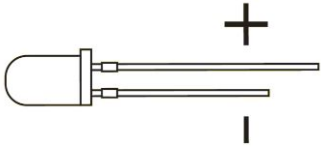1. You need: 1 LED light, copper tape, 1 battery
2. On the diagram to the left, place copper tape along all the lines on the (-) negative side. Make sure there are not breaks in the tape.
3. Place the battery negative side down where shown. Make sure it overlaps the copper tape.
4. Add copper tape to the positive (+) side of the circuit diagram all the way to the positive side of battery. Make sure to continue tape to cover battery.
5. Insert LED through the **FRONT** of the card with the longer wire (+) to the left. On inside of card, bend wires so the bulb is flat to the paper and the wires lay on top of the copper tape.
6. Add copper tape on top of the wires to secure.
7. Close card and press on "Happy Halloween." If your LED lights up, you are creating a closed circuit that allows electricity to pass from the battery to the LED!



+ Long side

- short side

+


- Negative side of battery:
Facing down covering the -
copper tape

Battery

Positive side of battery: Facing up with the + copper tape on top

Troubleshooting

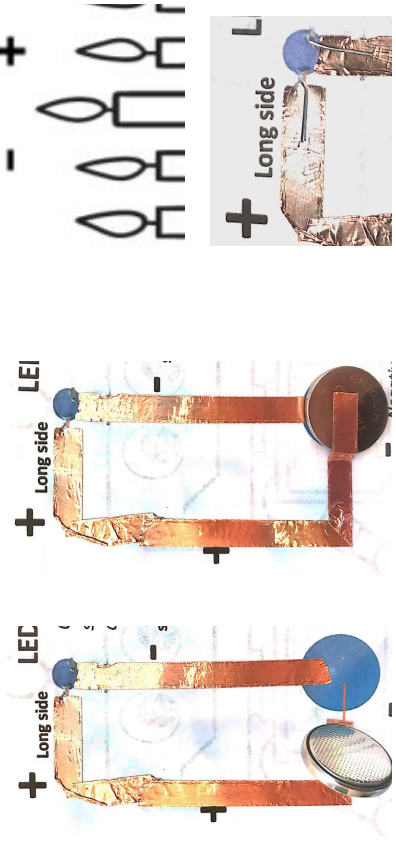1. Check LED and battery are working
2. Reverse battery
3. Make sure + and - copper tape strips are not touching
4. Make sure copper tape is continuous and smooth




Kwanzaa (Dec. 26 - Jan. 1) is an annual holiday that celebrates both African culture and Black heritage in the USA. While Kwanzaa is not an African holiday, it is inspired by many African cultural practices, using traditional woven mats called a *mkeka* (muh-KAY-kuh) having baskets filled with fruits and vegetables to represent the harvest and a unity cup called *kikombe cha umoja* (kee-KOHM-bee cha oo-MOH-jah) placed on it. The *kinara* (kee-NAH-ruh) holds seven candles: one black, three red, and three green. The black candle in the middle represents unity among people of African descent; the red candles on the left represent the past, and the green candles on the right stand for the future.

Learn more about Kwanzaa at

<https://kids.nationalgeographic.com/celebrations/article/kwanzaa>





www.vivifystem.com

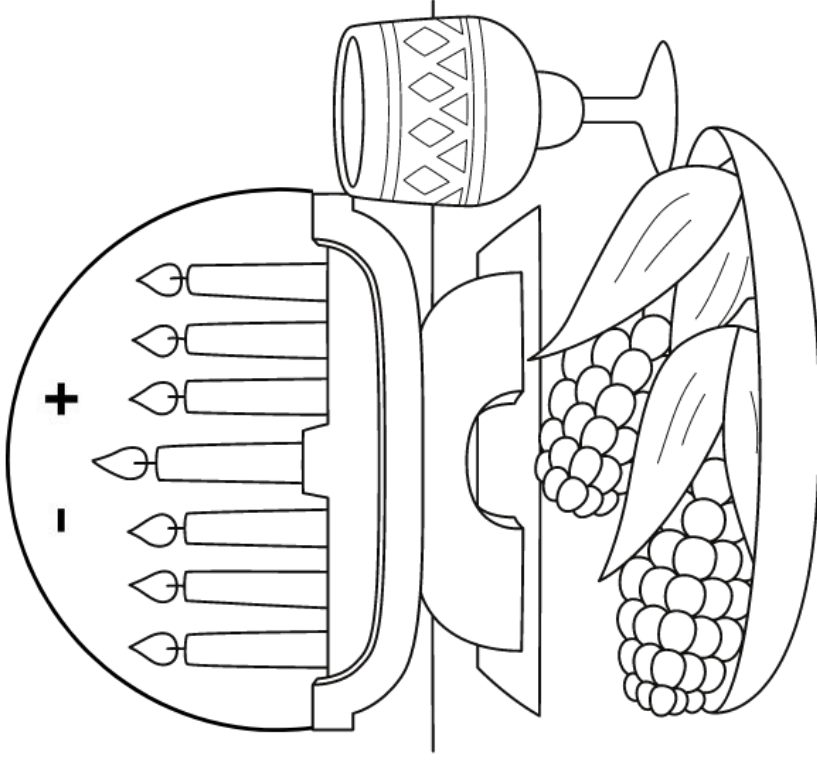

Joyous
KWANZAA

Ghost Circuit Instructions:

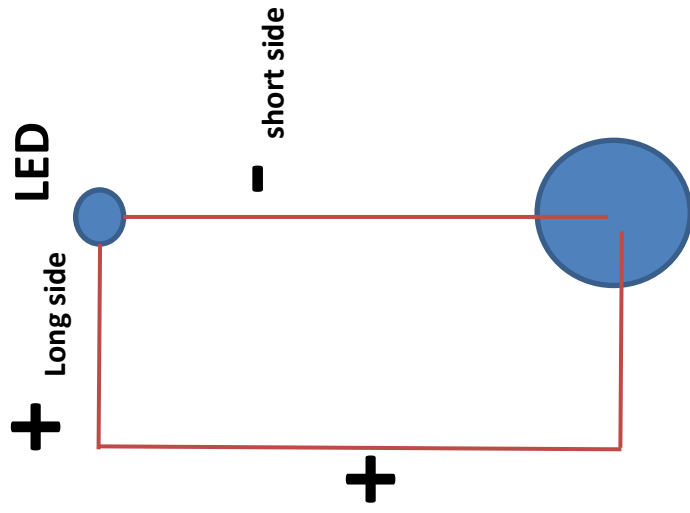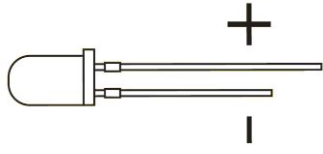1. You need: 1 LED light, copper tape, 1 battery
2. On the diagram to the left, place copper tape along all the lines on the (-) negative side. Make sure there are not breaks in the tape.
3. Place the battery negative side down where shown. Make sure it overlaps the copper tape.
4. Add copper tape to the positive (+) side of the circuit diagram all the way to the positive side of battery. Make sure to continue tape to cover battery.
5. Insert LED through the **FRONT** of the card with the longer wire (+) to the left. On inside of card, bend wires so the bulb is flat to the paper and the wires lay on top of the copper tape.
6. Add copper tape on top of the wires to secure.
7. Close card and press on "Happy Halloween." If your LED lights up, you are creating a closed circuit that allows electricity to pass from the battery to the LED!




Battery
Positive side of battery: Facing up with the + copper tape on top
Negative side of battery: Facing down covering the - copper tape


LED
Positive side of LED: Facing up with the + copper tape on top
Negative side of LED: Facing down covering the - copper tape

Troubleshooting

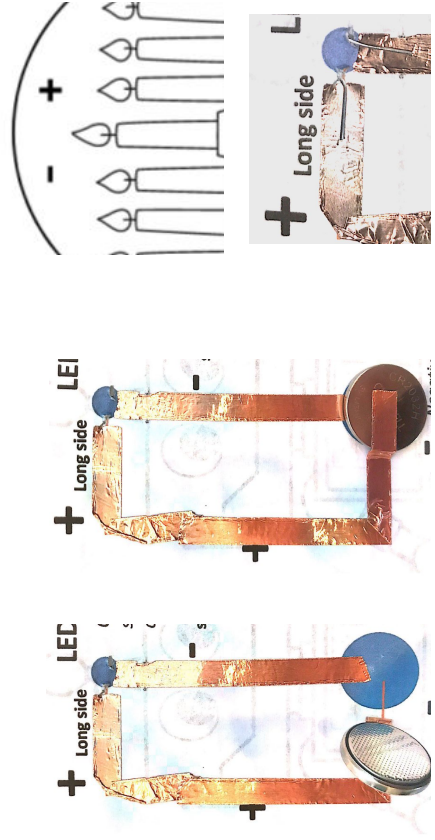1. Check LED and battery are working
2. Reverse battery
3. Make sure + and - copper tape strips are not touching
4. Make sure copper tape is continuous and smooth



STEM Family Night Station



STEM Family Night

BUNDLE!


Complete Planning Guide

14 STEM Activities & Station Handouts

vivify
VIVIFYSTEM.COM

This activity is a great station for a STEM Family Night! For a complete planning guide along with 14 stations, check out our STEM Family Night Guide and Activities [here](#).

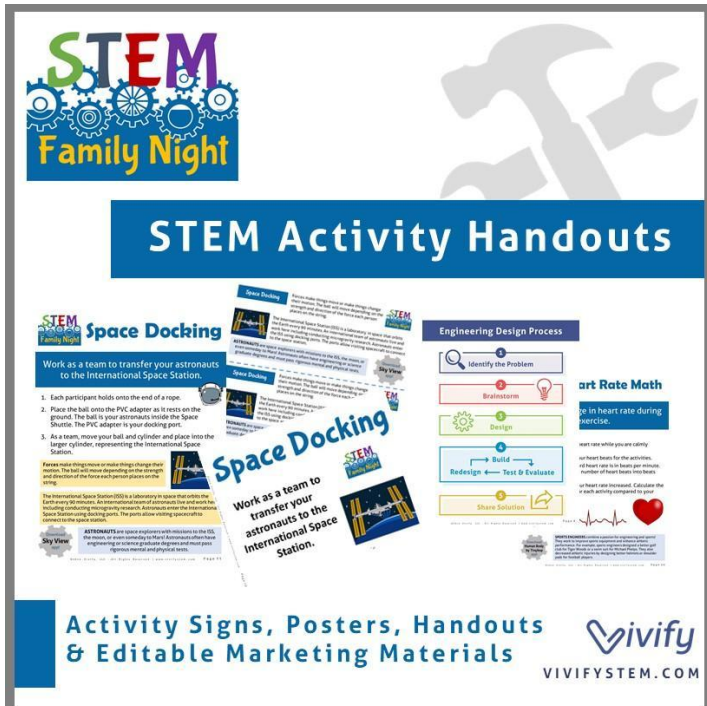Learn more about STEM Family Nights [here](#).



STEM Family Night

STEM Activity Handouts

Space Docking

Work as a team to transfer your astronauts to the International Space Station.

- Each participant holds onto the end of a rope.
- Place the ball onto the PVC adapter as it rests on the ground. The ball is your astronaut inside the Space Shuttle. The PVC adapter is your docking port.
- As a team, move your ball and cylinder and place into the larger cylinder, representing the International Space Station.

Heart Rate Math

Measure your heart rate during a 1-minute rest period. Then, measure your heart rate during a 1-minute exercise period. Calculate the difference between the two heart rates. This difference is your heart rate during exercise.

Build A Boat

Build a boat that can hold the most pennies.

Space Docking


Work as a team to transfer your astronauts to the International Space Station.

Landing Device

Build a device that can land a soft object safely.

Activity Signs, Posters, Handouts & Editable Marketing Materials

vivify
VIVIFYSTEM.COM

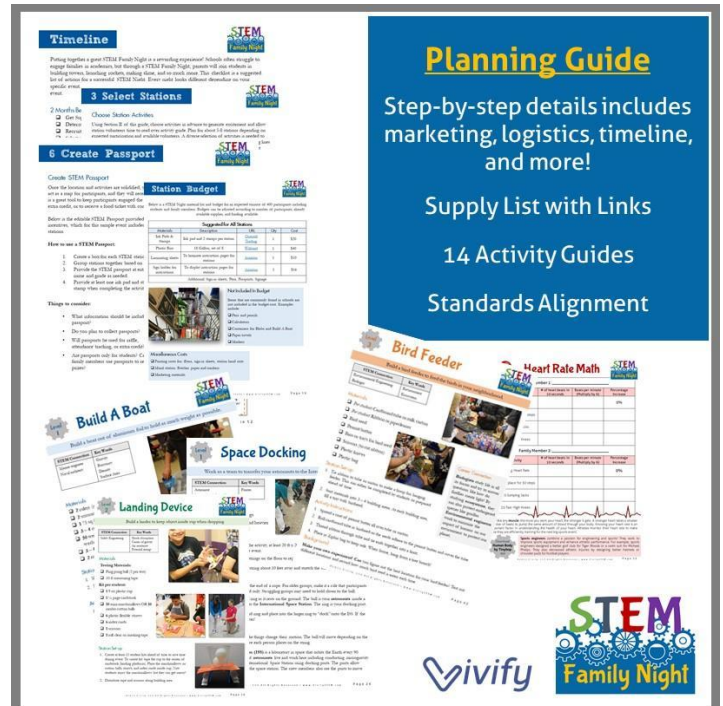

STEM Family Night

Planning Guide

Step-by-step details includes marketing, logistics, timeline, and more!

Supply List with Links

14 Activity Guides

Standards Alignment

Timeline

3 Select Stations

6 Create Passport

Station Budget

Station	Materials	Cost
Space Docking	String, Ball, PVC Adapter, PVC Cylinder	\$5.00
Heart Rate Math	Heart Rate Monitor, Stopwatch	\$10.00
Build A Boat	Aluminum Foil, Pennies, Rubber Band	\$5.00
Space Docking	String, Ball, PVC Adapter, PVC Cylinder	\$5.00
Landing Device	Straws, Paper, Tape	\$5.00

Bird Feeder

Heart Rate Math

vivify
STEM Family Night

Want more STEM?

For a complete list of all of Vivify STEM resources by topic and grade, go to:

<https://www.vivifystem.com/curriculum-map>



Help! I need to plan a year-long STEM class! What should I cover? What is appropriate for each grade level?

We can help! [Click here](#) for guidance on a scope and sequence of a STEM class plus resources and examples for planning a STEM curriculum map.



3 Stages of STEM

STEM generally revolves around the Engineering Design Process that embraces failure, relies on teamwork, and requires critical thinking and creativity. While exciting, educators often become intimidated as a search for curriculum leads to an overwhelming range of activities from index towers to robotics competitions. At Vivify, we believe that not all STEM is created equal. Educators should adopt a [3 Stages of STEM](#) approach by progressively building towards more complex projects.

Click images for lessons for each stage!

